

The background of the top section is a blue gradient with white line-art illustrations of various electronic components, including capacitors, diodes, and integrated circuits.

Technical Article

Eliminating snubber circuits in AC/DC power supplies through the use of silicon carbide diodes

Silicon carbide diodes have been around for some time now but have had little take-up in power supplies due to their relatively high cost. XP Power has recently adopted a silicon carbide (SiC) diode for the first time in the design of its latest family of modular, configurable power supplies known as fleXPower.




T H E X P E R T S I N P O W E R

The company's previous generation of configurable power supplies, the LP and MP series, used conventional diodes as boost converter rectifiers. The challenge with conventional diodes in boost converters is the high reverse current. This creates wasted power in the diode and switching transistor because the energy in the reverse current spikes needs to be dissipated using a snubber circuit.

Six additional components – 2 diodes, two capacitors, a resistor and an inductor – are used to dissipate the power generated by the unwanted reverse current. The resulting PCB board area is shown in Figure 1, the relevant components are highlighted with blue dots.

Figure 1

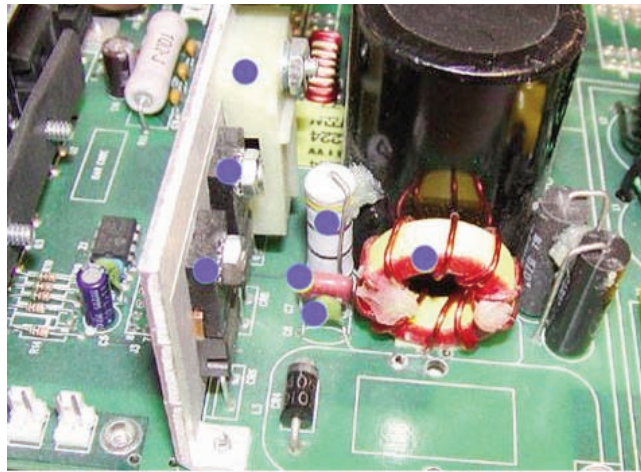

The SiC diode has very low reverse current so can be used without additional components, resulting in space saving on the board (as shown in Figure 2), lower assembly costs and greater reliability. In addition, because almost no power is lost due to reverse current, the efficiency of the power supply is increased by around 1% - a significant improvement.

Figure 2



With respect to cost, the SiC solution is now comparable to using a conventional diode and snubber circuit. Estimates of component costs used based on XP Power's 1000 W MP series power supply are shown in Table 1.

The lower component cost of the conventional solution is compensated for by lower assembly costs for the power supply. Furthermore, the price of SiC diodes from the main manufacturers, Infineon and Cree, is continuing to fall as the technology becomes more widely adopted. In conclusion, using SiC diodes is now comparable in overall cost to using conventional boost rectifiers, with the added benefits of improved power supply efficiency, space saving and enhanced reliability due to the reduced component count.

Conventional diode and snubber		Silicon carbide diode	
Component	Cost (US\$)	Component	Cost (US\$)
D1 20A/600V diode	1.75	D1 SiC diode 12A	4.80
D2 Diode	0.70		
D3 Diode	0.70		
L inductor	0.17		
R resistor	0.03		
C1 capacitor	0.09		
C2 capacitor	0.06		
TOTAL	3.50	TOTAL	4.80

Table 1

www.xppower.com

North American HQ

XP Power
990 Benecia Avenue, Sunnyvale, CA 94085
Phone : +1 (408) 732-7777
Fax : +1 (408) 732-2002
Email : nasales@xppower.com

North American Sales Offices

Toll Free.....+1 (800) 253-0490
Central Region.....+1 (972) 578-1530
Eastern Region+1 (973) 658-8001
Western Region.....+1 (408) 732-7777

European HQ

XP Power
Horseshoe Park, Pangbourne,
Berkshire, RG8 7JW, UK
Phone : +44 (0)118 984 5515
Fax : +44 (0)118 984 3423
Email : eusales@xppower.com

German HQ

XP Power
Auf der Höhe 2, D-28357
Bremen, Germany
Phone : +49 (0)421 63 93 3 0
Fax : +49 (0)421 63 93 3 10
Email : desales@xppower.com

European Sales Offices

Austria+41 (0)56 448 90 80
Belgium+33 (0)1 45 12 31 15
Denmark+45 43 42 38 33
Finland.....+46 (0)8 555 367 01
France+33 (0)1 45 12 31 15
Germany.....+49 (0)421 63 93 3 0
Italy+39 039 2876027
Netherlands+49 (0)421 63 93 3 0
Norway.....+47 63 94 60 18
Sweden +46 (0)8 555 367 00
Switzerland..... +41 (0)56 448 90 80
United Kingdom.....+44 (0)118 984 5515

Global Catalog Distributors

AmericasNewark newark.com
Europe & Asia.....Farnell farnell.com
China.....Premier Electronics premierelectronics.com.cn

Asian HQ

XP Power
401 Commonwealth Drive, Haw Par Technocentre, Lobby B,
#02-02, Singapore 149598
Phone : +65 6411 6900
Fax : +65 6741 8730
Email : apsales@xppower.com
Web : www.xppowerchina.com / www.xppower.com

Asian Sales Offices

Shanghai +86 21 51388389
Singapore..... +65 6411 6902

Distributors

Australia+61 2 9809 5022 Amtex
Balkans+386 1 583 7930 Elbacomp
Czech Rep.+420 235 366 129 Vums Powerprag
Czech Rep.+420 539 050 630 Koala Elektronik
Estonia+372 6228866 Elgerta
Greece+30 210 240 1961 ADEM Electronics
Israel+972 9 7498777 Appletec
Japan+81 48 864 7733 Bellnix
Korea+82 31 422 8882 Hanpower
Latvia+371 67501005 Caro
Lithuania.....+370 5 2652683 Elgerta
Poland.....+48 22 8627500 Gamma
Portugal.....+34 93 263 33 54 Venco
Russia+7 (495)234 0636 Prosoft
Russia+7 (812)325 5115 Gamma
South Africa.....+27 11 453 1910 Vepac
Spain.....+34 93 263 33 54 Venco
Taiwan+886 3 3559642 Fullerton Power
Turkey+90 212 465 7199 EMPA



T H E X P E R T S I N P O W E R